

PAPER ID : 2018

TEE-201/TEE-101

Printed Pages : 3

Paper ID and Roll No. to be filled in your Answer Book

Roll No.

**B. Tech.**

(SEM. II) EXAMINATION, 2010

**ELECTRICAL ENGG.**


Time : 3 Hours]

[Total Marks : 100

**Note :** Attempt all questions. All questions carry equal marks.

1. Attempt any **Four** Parts : 5×4=20

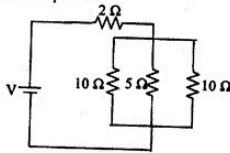- (a) Define Resonance and Quality factor for the ac circuit.
- (b) State and explain the Theenin's theorem.
- (c) In the circuit shown below, determine the constant voltage  $V$  if the current in the  $5\ \Omega$  resistor is 14 amperes.



- (d) Draw the phasor diagram, showing voltages and currents, if a sinusoidal voltage is applied to (i) R (ii) R-L (iii) R-C (iv) C-L (v) R-L-C circuits.
- (e) Explain the conversion of Current source to Voltage source and vice versa.
- (f) Explain the meaning of unilateral and bilateral elements.


2018]

1

[Contd...

2 Attempt any **four** parts : 5×4=20

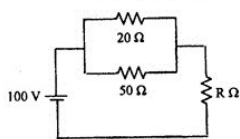- (a) Determine the value of the resistance R shown below if the potential drop across it is 25 Volts.



- (b) An iron ring of mean length 50 cm has an air gap of 1 mm and a winding of 100 turns. If the relative permeability of iron is 300 and a current of 1 A flows through the coil. Calculate the flux density. Neglect fringing.
- (c) A rectangular coil of 1000 turns, when carrying a certain current produces a flux of 4.5 mWb. Calculate the average value of induced emf if this current through the coil is reversed in 100 milliseconds.
- (d) Explain the magnetization curve of a magnetic material. Properly label it.
- (e) Explain the Peak factor and Form factor in ac quantities
- (f) Explain the Real and reactive power in ac circuits

3 Attempt any **two** parts : 2×10


- (a) Define the term Voltage Regulation in case of single phase transformers. Derive the condition for maximum voltage regulation.
- (b) The diagram shows the equivalent circuit for a single phase transformer. Figure given are of resistances and reactances in ohms in terms of the primary side. The ratio of secondary to

2018]

2

[Contd...

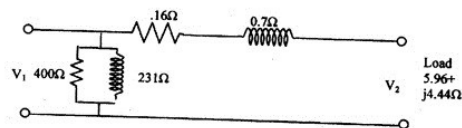primary turns is 10 and the load is inductive. Find : (a) the secondary terminal voltage; (b) the primary current; (c) the efficiency, if the applied voltage is 220 V.



- (c) What types of losses occurs in the transformer? Explain the methods to reduce them.

4 Attempt any **two** parts : 2×10

- (a) Explain the working principle of moving iron instruments.
- (b) Why starters are used to start an Induction motor? List all the methods could be adopted for starting an induction motor. Explain any one method.
- (c) What do you mean by damping torque? List all the methods to attain this torque and explain one of them.

5 Attempt any **two** parts : 2×10

- (a) Prove that torque in a D. C. motor is given by  $T_e = K_a \phi I_a$ , where all terms have their usual meanings.
- (b) Find the minimum number of poles for a 1200 kW generator if the average voltage between Commutator segments is not to exceed 15 V and the armature ampere turns per pole not exceed 10,000.
- (c) Explain the voltage buildup phenomena in a D.C. shunt generator.

2018]

3

[ 3980 ]