

**B. TECH. Ist - Year**

FIRST SEMESTER EXAMINATION, 2007-2008

**TEC-101 BASIC ELECTRONICS**

Time : 3 Hours


Maximum Marks : 100

**Note :** Attempt any FIVE questions.

1. (a) Explain graphically, why the energy levels of an atom become energy bands in a solid. Show the variation of energy levels with atomic distance. (5)
  - (b) On the basis of energy band gap theory, explain the formation of valence band. Differentiate among conductors, insulators and semiconductors. (5)
  - (c) Reverse saturation current of a Si Diode is  $0.3 \mu\text{A}$ . Calculate its forward resistance at an applied voltage of 1 V. (5)
  - (d) Determine the rating of a transformer secondary to deliver a 100 W of dc power to a load under full-wave and half-wave rectifiers. (5)
2. (a) Define the following terms :
    - (i) Knee voltage
    - (ii) Peak Inverse voltage
    - (iii) Reverse saturation current
    - (iv) Breakdown voltage
    - (v) Ideal diode(10)
  - (b) Determine ac resistance for a semiconductor silicon diode having forward bias of 200mV and reverse saturation current of  $1 \mu\text{A}$  at room temperature. (5)
  - (c) Explain the break mechanism which occurs in Zener diode. (5)

3. (a) What are clipping circuits? Draw the output waveform for positive and negative clippers if the input is sinusoidal. Also explain the operation of combinational clipper for a square input. (10)

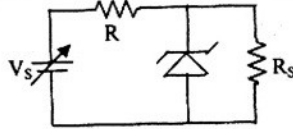- (b) Draw the V-I characteristics of a zener diode and explain how does a zener regulate a voltage. The input voltage for the figure shown below varies from 35 to 45 volt,  $V_Z = 20$  V,  $r_z = 5$  ohm,  $I_{L(\min)} = 0$  mA,  $I_{L(\max)} = 100$  mA,  $I_{Z(\min)} = 10$  mA,  $I_{Z(\max)} = 400$  mA. Find the value of  $R_L$ , R and  $P_{Z(\max)}$ . (10)



4. (a) Draw and explain the input and output characteristics of a BJT in CE configuration, indicating the operating regions. Derive the relationship between  $\alpha$ ,  $\beta$  and  $\gamma$ . Explain why CE configuration is most widely used in amplifier circuits. (10)
- (b) Determine pinch off voltage, amplification voltage and drain resistance of FET. Explain the volt ampere characteristics of FET. Using suitable circuit arrangement, derive the relationship  $\mu = r_d \times g_m$ . (10)
5. (a) What is significant difference between the construction of an enhancement type MOSFET and depletion type MOSFET? Explain with suitable diagram. (7)
- (b) Differentiate between BJT and FET. What are the advantages of the FET over a conventional BJT? (7)

- (c) Draw the ac equivalent circuit of a common source amplifier, and find the expression for voltage gain. (6)

6. (a) Perform the following conversions :

(i)  $(1BE)_{16} = ( )_8$

(ii)  $(676)_8 = ( )_2$

(iii)  $(321)_4 = ( )_{10}$

(iv)  $(10101.001)_2 = ( )_8$  (6)

- (b) Add and subtract the following numbers without converting to decimal numbers :

$(4F3A)_{16}$  and  $(23C1)_{16}$  (7)

- (c) Minimize the following Boolean function using K-map :

$$F = \overline{W}(\overline{xy} + \overline{xy} + xyz) + \overline{xz}(y + w)$$

$$d = \overline{wx}(\overline{yz} + \overline{yz}) + wyz$$

- Also find the POS from the above simplified Boolean expressions. (7)

7. (a) List any five ideal characteristics of an operational amplifier. Also define the following terms :-

- (i) CMRR (ii) slew rate (iii) PSRR (iv) input offset voltage. (10)

- (b) Explain, with the help of a neatly labeled circuit diagram, how an amplifier can be used as

- (i) Differentiator, (ii) Integrator, (iii) Adder and (iv) Difference Amplifier. (10)