

Roll No. :

--	--	--	--	--	--	--	--	--	--

No. of Printed pages - 02

B.TECH
THIRD SEMESTER EXAMINATION 2008-09
TEC 304, PULSE AND DIGITAL ELECTRONICS

- 1 a) Simplify the following by using Tabular method: (10)
 $F(w,x,y,z) = \Sigma (2,3,12,13,14,15)$
b) What is the difference between Asynchronous and Synchronous counter. Explain the 4-bit ripple counter. (10)
- 2 a) Implement the following function by using multiplexer (10)
 $F(A,B,C,D) = \Sigma(1,3,5,6,10,12,13,14,15)$
b) What is the race – around condition? Explain the working between of master- slave flip flop. (10)
- 3 Define any four (10)
 - a) Figure of merit
 - b) Fan out
 - c) Noise immunity
 - d) Demultiplexer
 - e) Encoder
- 4 a) What do you mean by voltage regulator? Explain the operation of shunt- voltage regulator. (10)
b) Explain the op- amp configured first ordered low pass butterworth filter and find out the pass band gain (10)
- 5 a) What is the response sinusoidal input for low pass RC circuit. How a low pass circuit act as a integrator? (10)
b) Draw and explain functional diagram of 555 timer .explain the monostable mode of Ic 555 timer. (10)
- 6 a) Explain a 4 bit R-2R ladder type D/a convertor in detail. Explain the simultaneous type A/D converter. (10)
b) A certain memory has capacity of 16K x 32. Find out the following (10)
 - i) Number of Address lines
 - ii) Number of output lines
 - iii) Number of memory locations
 - iv) Number of bits stored in the memory.

[Turn over

- 7 a) Describe the difference between a bipolar integrated circuit and MOS integrated circuit. Draw and explain the working of CMOS NAND circuit. (10)
- b) Attempt any four: (10)
- i) Ring counter
 - ii) Schmitt trigger
 - iii) Magnitude comparator
 - iv) Static and dynamic memory
 - v) VCO
 - vi) Astable and Monostable multivibrator
