

Roll No. to be filled in your Answer Book

Roll No.

--	--	--	--	--	--	--	--	--	--	--

Semester: III

B. Tech End Semester Examination Dec 2014

NETWORK ANALYSIS AND SYNTHESIS

Time: 3 Hours

MM. 100

Note:- Attempt All Questions. All Questions carry equal marks.

Q1. Attempt any four Questions of the following:- 4x5=20

- Define the terms: Tree, Co-tree, Tie-set & Cut-set.
- Explain the concept of duality with the help of suitable example.
- Write the matrix-node equation using the nodal analysis & the matrix-loop equation using the loop analysis in graph theory
- Calculate & draw the total number of possible trees for the given reduced incidence matrix:

$$A = \begin{bmatrix} 1 & 0 & 0 \\ -1 & 0 & -1 \\ 0 & 1 & 1 \end{bmatrix}$$

- The Z parameters of a circuit are given by  $\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$  obtain transmission line parameters
- Define the following terms related to a network graph
  - Path
  - Loop
  - Tree
  - Cotree
  - Planar Graph

(1)



**Q2. Attempt any four Questions of the following:- 4x5=20**

- Determine the condition of reciprocity and symmetry in h parameters.
- Check when the function  $Z(s) = \frac{2s^2+2s+1}{s^3+s^2+s+2}$  is a positive real function
- Discuss the properties of RC Driving point impedance.
- State & prove compensation theorem with the help of a suitable example.
- Define the terms Gain Margin and Phase margin.
- State & prove Milliman's theorem for AC voltage sources.

**Q3. Attempt any two questions of the following 2x10=20**

- For the symmetrical 2-port network shown in Fig.2, find the z-and ABCD-parameters.

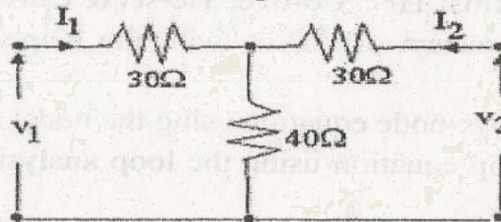


Figure 2

- Find the driving-point impedance  $Z(s) = K \cdot \frac{N(s)}{D(s)}$ , for the network shown in Fig.3. Verify that  $Z(s)$  is positive real and that the polynomial  $D(s) + K.N(s)$  is Hurwitz.

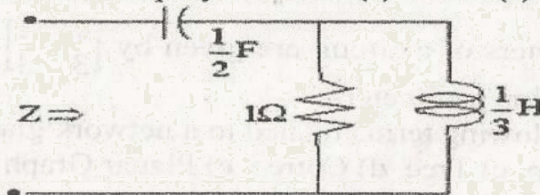



Figure 3.

(2)

(c)

Q5. Attempt any two questions of the following  $2 \times 10 = 20$

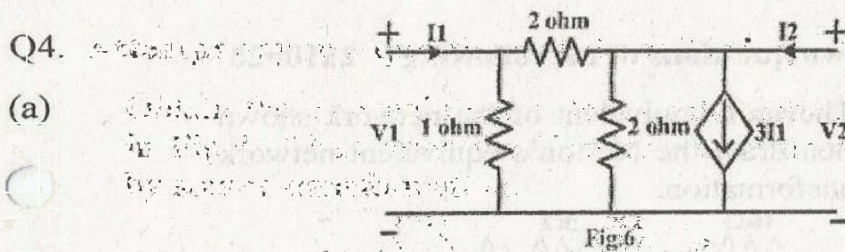- (a) Obtain Z-parameters of the network shown in fig.6. Whether the network shown is symmetrical & reciprocal or not.



- (b) Consider the function  $F(s) = \frac{s^2 + 1.03}{s^2 + 1.23}$ . Plot its poles and zeroes. Sketch the amplitude and phase for  $F(s)$  for  $1 \leq \omega \leq 10$ .

- (c) Given  $F(s) = \frac{6(s+2)(s+4)}{s(s+3)}$ , find the continued fraction expansion & hence synthesize the network for the case when:
- $F(s)$  is an impedance  $Z(s)$ .
  - $F(s)$  is an admittance  $Y(s)$ .

(c)

For the network function

$$F(s) = \frac{2s^2 + 1}{s^2 + 3}$$

Sketch the amplitude and phase plots of  $F(s)$  for  $1 \leq \omega \leq 10$ .

(4) TEE-301 // 1750 // 4

(2)